

Chapter 6: Sequential Circuits

时序逻辑电路

Dr Guohun Zhu

Email: g.zhu@uq.edu.au or guohun.zhu.phd@ieee.org

Presentation Outline

- ❖ Introduction to Sequential Circuits
- ❖ Synchronous versus Asynchronous (同步 vs 异步)
- ❖ Review Latches
- ❖ Review Flip-Flops
- ❖ Characteristic Tables and Equations

Reference

❖ Digital Electronics Principles and Applications by

Roger L. Tokheim

❖ Sequential logic

- https://github.com/computation-structures/course/blob/main/lectures/L05_Sequential_Logic.md

❖ Digital design source code

- <https://github.com/hneemann/Digital>
-

The Classes of Digital Circuits

- ❖ Two classes of digital circuits. (两类数字电路)

 - ◇ Combinational Circuits


 - ◇ Sequential Circuits

- ❖ Combinational Circuits (组合电路)

 - ◇ $O = F(x)$

 - ◇ Function of Inputs only

 - ◇ NO internal memory (没有内部存储)

 


- ❖ Sequential Circuits (时序电路)

 - ◇ $O = F(x, ?)$

 - ◇ Have memory ability (有记忆能力)

A Sequential Logical Example

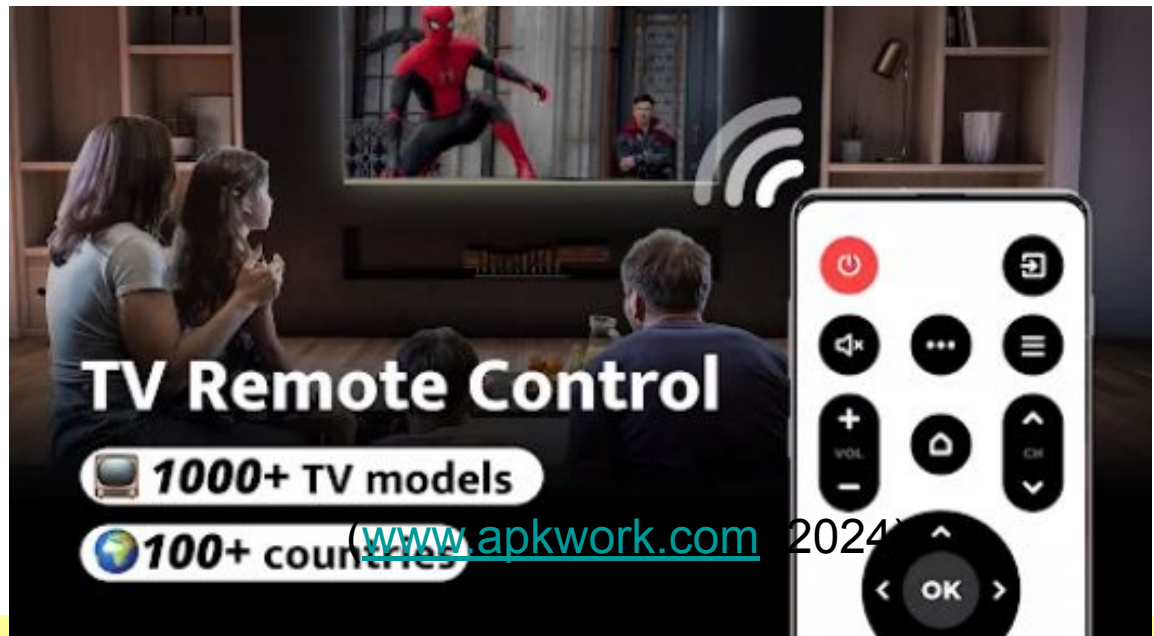- ❖ TV Remote Control with Channel Up and Channel Down Buttons
 - ◇ What is the next channel if press “Channel Up” Button?
 - ◇ If current channel number : 8, then next channel ?
 - ◇ If current channel number : 6, then next channel ?
 - ◇ The remote control's output is dependent on its previous state(O_0)
 - ◇ and **Buttons: x**
 - ◇
 - ◇ $O_1 = F(x, O_0)$



Introduction to Sequential Circuits


A Sequential circuit consists of: (Text books page 247)

1. Memory elements:

- ◇ Latches or Flip-Flops
- ◇ Store the **Present State: S**

 2. Combinational Logic

- ◇ Computes the **Outputs** :O
- ◇ Computes the **Next Activity State** : E



Both O, E depends on the Inputs and the Present State Q

However, S could be affected by **E and** the memory (old S)


时序电路的描述方式：逻辑方程

Text book page 247


输出方程： $O=f_1(X, S)$

激励方程 $E=f_2(X, S)$

状态方程 $S_{n+1}=f_3(E, S_n)$

 

A Counter Example

 

Counter increase one when a pulse signal was obtained. If there has no pulse, the state has no changed.

The pulse is called a **clock**

Assume that the output and all states change simultaneously: **Synchronous** (同步)

Output and States are changed at any time. **Asynchronous** (异步)

Two Types of Sequential Circuits

1. **Synchronous** Sequential Circuit

同步时序电路

◇ Uses clock signals as additional inputs

- single-clock synchronous

单时钟同步


- Multiple clock signals is possible, but analyzing (the timing) is quite tricky

◇ Changes in the memory elements are controlled by the clock

◇ Changes happen at discrete instances of time

变化发生在离散的时间点

Model: Discrete Time

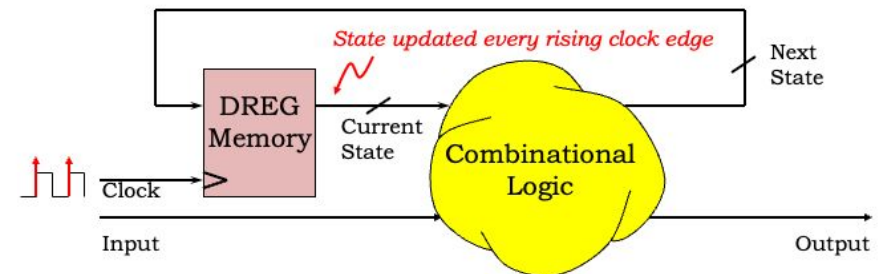


Active Clock Edges punctuate time ---

- Discrete Clock periods
- Sequences of states
- Simple rules – eg truth tables – relating outputs to inputs and the current state)
- ABSTRACTION: Finite State Machines (next lecture!)

抽象化: 有限状态机

 2. Asynchronous Sequential Circuit

- ◇ No clock signal
- ◇ Changes in the memory elements can happen at any instance of time
- ◇ Example: SR Latch (SR锁存器)




S-R Latch 功能表

S_L	R_L	Q	Q_N
1	1	维持现态	
1	0	0	1
0	1	1	0
0	0	1*	1*

❖ Advantage and Drawbacks


- ◇ Faster as there has no clock
- ◇ Difficult to design and analyze than synchronous sequential circuits

Synchronous Sequential Circuits

 

- ❖ Synchronous sequential circuits use a **clock signal**
- ❖ The clock signal is an input to the memory elements
- ❖ The clock determines **when** the memory should be updated
- ❖ The **present state** = output value of memory (stored)
- ❖ The **next state** = input value to memory (not stored yet)

The Clock

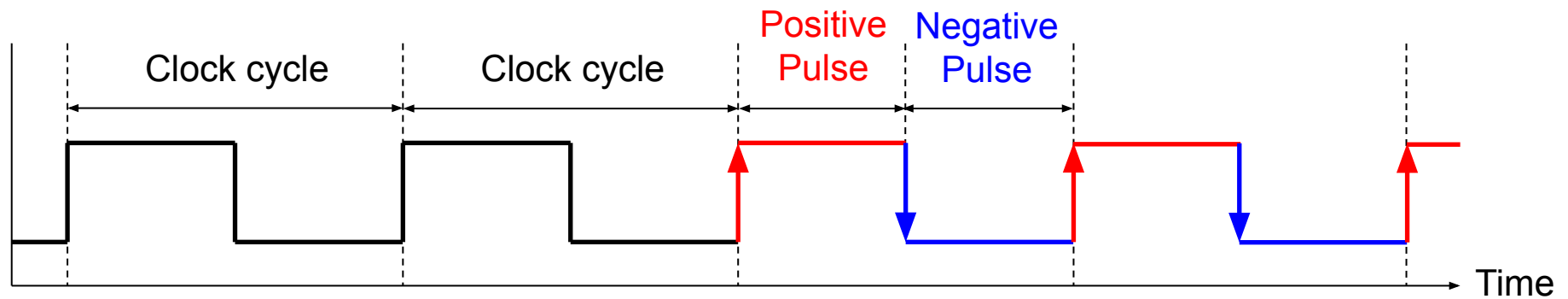

- ❖ Clock is a periodic signal 时钟是周期信号
- ❖ **Positive Pulse**: when the level of the clock is **1** 正脉冲
- ❖ **Negative Pulse**: when the level of the clock is **0** 负脉冲
- ❖ **Rising Edge**: when the clock goes **from 0 to 1** 上升沿
- ❖ **Falling Edge**: when the clock goes **from 1 down to 0** 下降沿

Memory Elements


- ❖ Memory can store and maintain binary state in electronically
 - ◇ 1-bit data: 0 or 1
- ❖ Alternative memory styles (其他存储形式)
 - ◇ Magnetic(磁性), optical (光学), or acoustic (声学)
 - ◇ Quantum memory (量子存储): qubits (量子位)
- ❖ Two main types:
 - ◇ Latches : level-sensitive (锁存器是电平敏感)
 - ◇ Flip-Flops : edge-sensitive (触发器是边沿敏感)
- ❖ Flip-Flops are used in synchronous sequential circuits
- ❖ Flip-Flops are built with latches

Next . . .

- ❖ Introduction to Sequential Circuits
- ❖ Synchronous versus Asynchronous
- ❖ **Review Latches**
- ❖ Review Flip-Flops
- ❖ Characteristic Tables and Equations



Review SR Latch

 - ❖ A **latch** is a memory element that can store 0 or 1
- ❖ An **SR Latch** can be built using two **cross-coupled** NOR gates (或非门)
- ❖ 请问能否用 NAND gates 建成 **SR Latch**?
- ❖ Two inputs: S (Set) and R (Reset)
- ❖ Two outputs: Q and \bar{Q}




SR Latch Operation



Set Operation

  


Store Operation

 

Reset Operation

 
 


Store Operation

 


SR Latch Invalid Operation


Invalid Operation

  


Race Condition

 


S = R = 1 should never be used

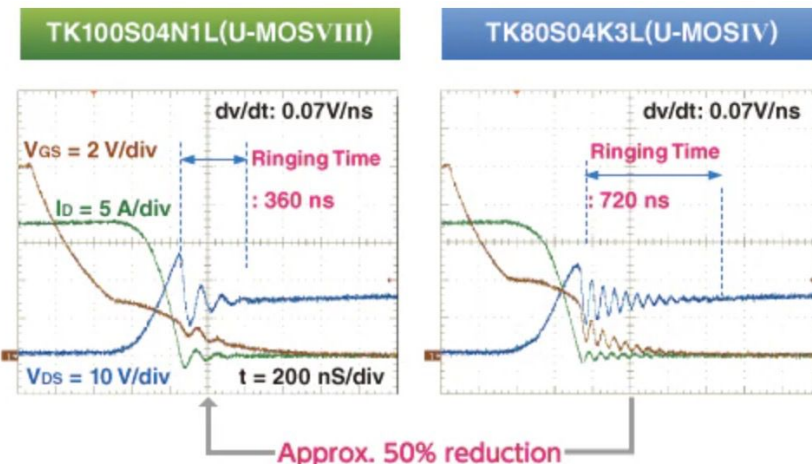

Unknown State

 


Timing Diagram of an SR Latch (时序图)

 


(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

 

Gated SR Latch with Clock Enable

 


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

- ❖ An additional Clock (enable) input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the S and R inputs have no effect on the latch
The latch will remain in the same state, regardless of S and R
- ❖ When **C=1**, then normal SR latch operation


Timing Diagram of an SR Latch with Enable

请补充完整时序(波形)图

 


Timing Diagram of an SR Latch with Enable

答案:

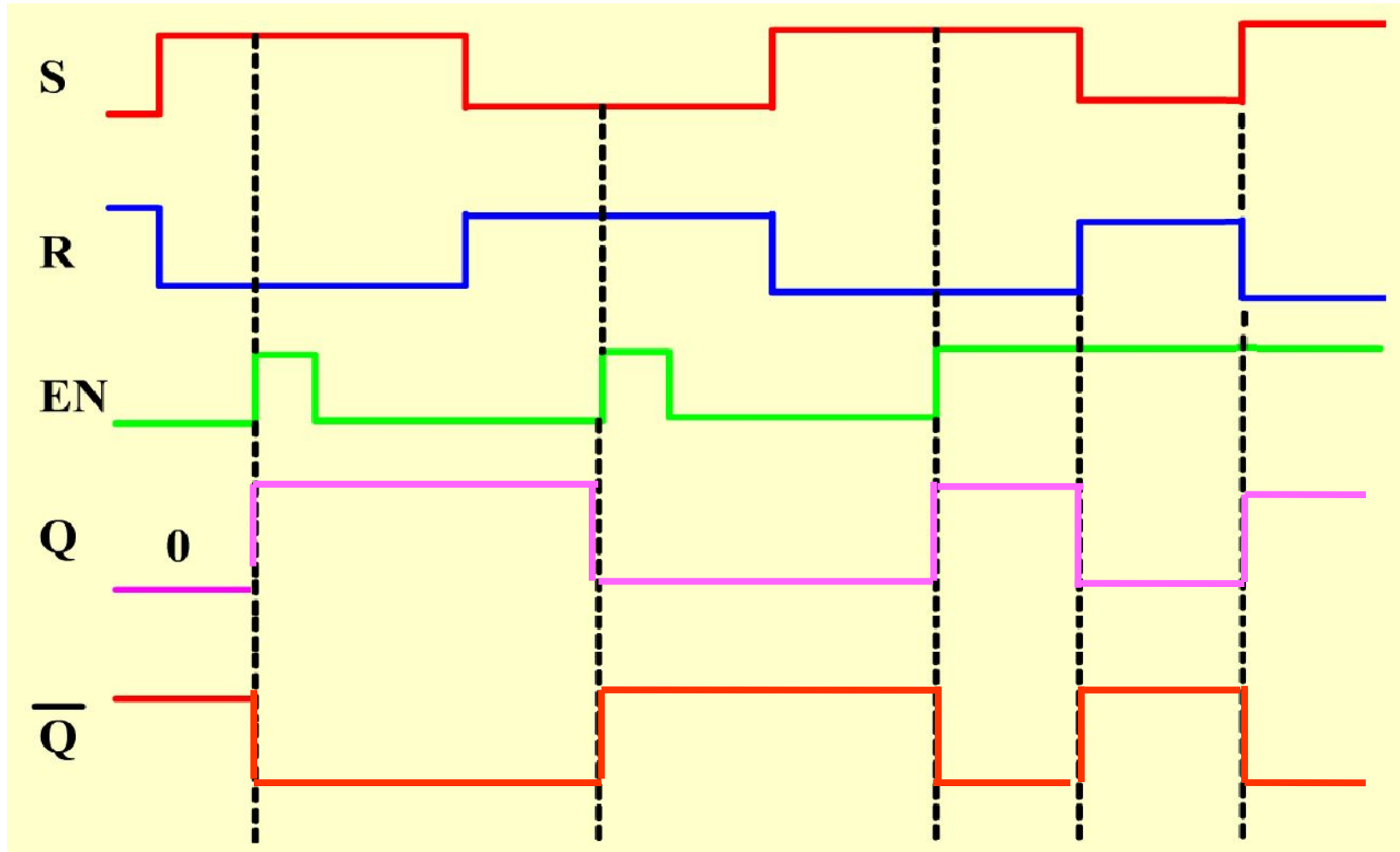

$\bar{S} \bar{R}$ Latch with NAND Gates


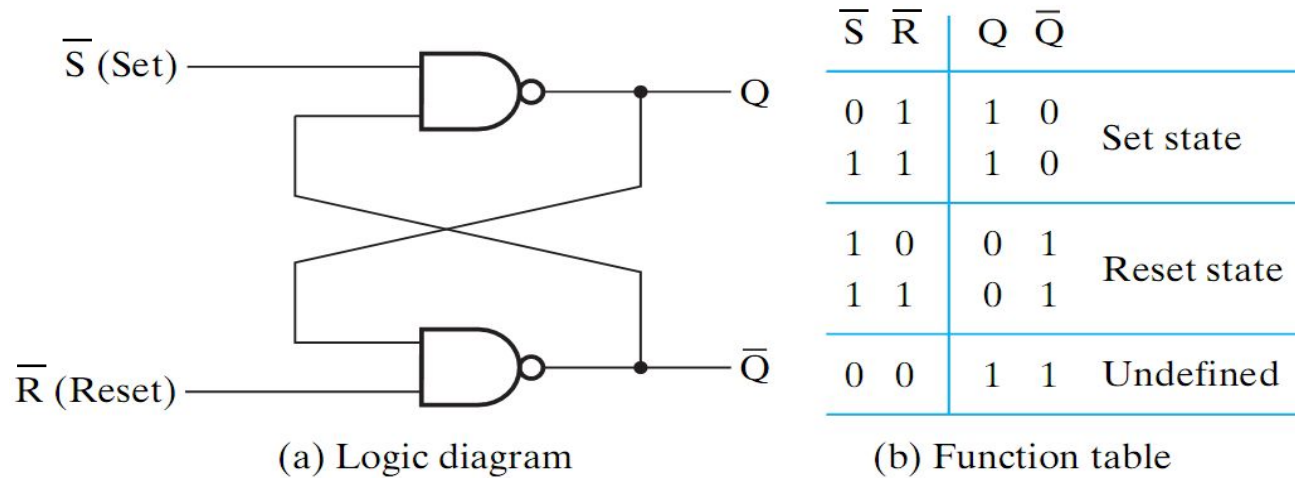


Known as
the Latch


- ❖ If $\bar{S}=?$ and $\bar{R}=?$ then **Set** ($Q=1$)
- ❖ If $\bar{S}=?$ and $\bar{R}=?$ then **Reset** ($Q=0$)
- ❖ When $\bar{S}=\bar{R}=?$, and Q is unchanged (remain the same)
- ❖ The latch stores its outputs Q and \bar{Q} as long as $\bar{S}=\bar{R}=?$
- ❖ When $\bar{S}=\bar{R}=?$ and Q is undefined (should never be used)

$\overline{S} \overline{R}$ Latch Operation



Set Operation

  


Store Operation

 

Reset Operation

 
 


Store Operation

 


\overline{S} \overline{R} Latch Invalid Operation

Invalid Operation

  

Race Condition

 


$\overline{S} = \overline{R} = 0$ should never be used


If \overline{S} and \overline{R} change from 0 \rightarrow 1 simultaneously then race condition (oscillation) occurs

Final Q and \overline{Q} are unknown

Unknown State

 


Gated SR Latch with Clock Enable

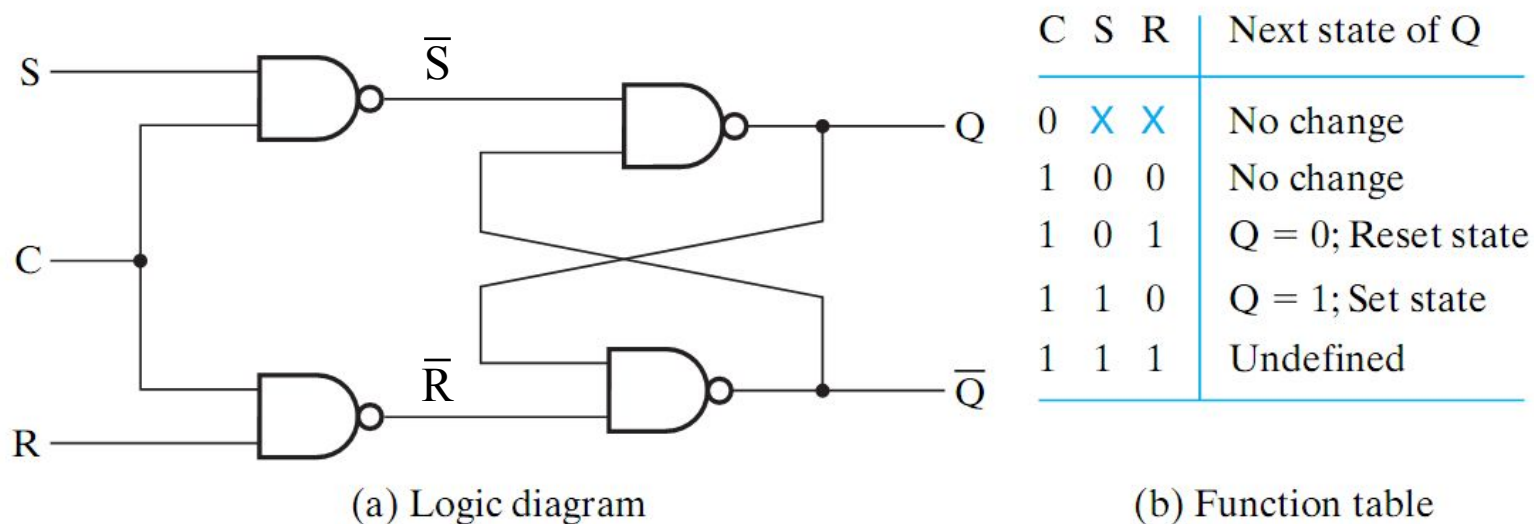

- ❖ An additional Clock (enable) input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the latch remains in the same state
- ❖ When **C=1**, then normal latch operation

The NAND gates invert the **S** and **R** inputs when **C=1**

D-Latch with Clock Enable

 


(a) Logic diagram


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

(b) Function table

C	D	S	\bar{R}	\bar{S}	R
1	0	0	1	1	0
1	1	1	0	0	1

 


Timing of a D-Latch with Clock Enable

 


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

Function table

 

Graphic Symbols for Latches

 

- ❖ A bubble appears at the complemented output \bar{Q}
Indicates that \bar{Q} is the complement of Q
- ❖ A bubble also appears at the inputs of an $\bar{S}\bar{R}$ latch
Indicates that **logic-0** is used (not logic-1) to set (or reset) the latch (as in the NAND latch implementation)


D-Latch Funtion

D-Latch: 只有一个数据输入端D 称为D锁存器, 也称为透明锁存器

状态转移真值表

D	Q^{n+1}
0	0
1	1

逻辑符号

 


特征方程: $Q^{n+1} = D (C=1)$

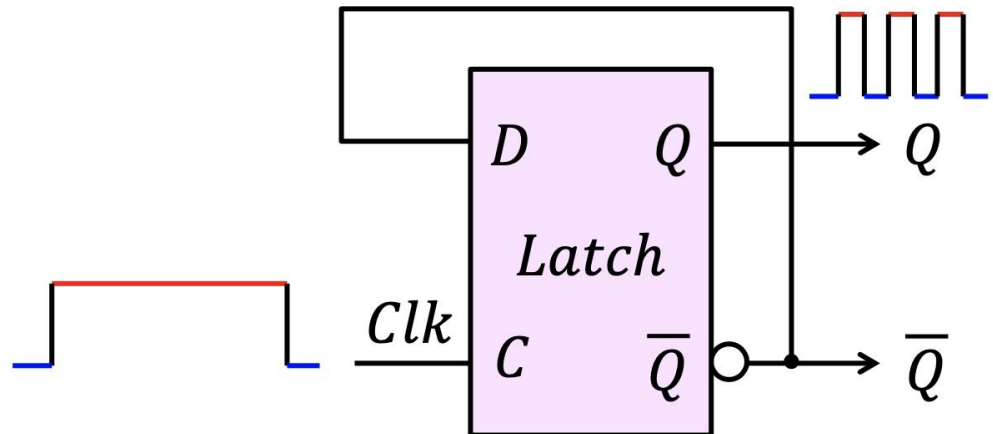
Problem with Latches

- ❖ A latch is **level-sensitive** (sensitive to the level of the clock)
- ❖ As long as the clock signal is **high** ...
Any change in the value of input D appears in the output Q
- ❖ Output Q keeps changing its value during a clock cycle
- ❖ Final value of output Q is uncertain

Due to this uncertainty,
latches are NOT used
as memory elements in
synchronous circuits



Home work

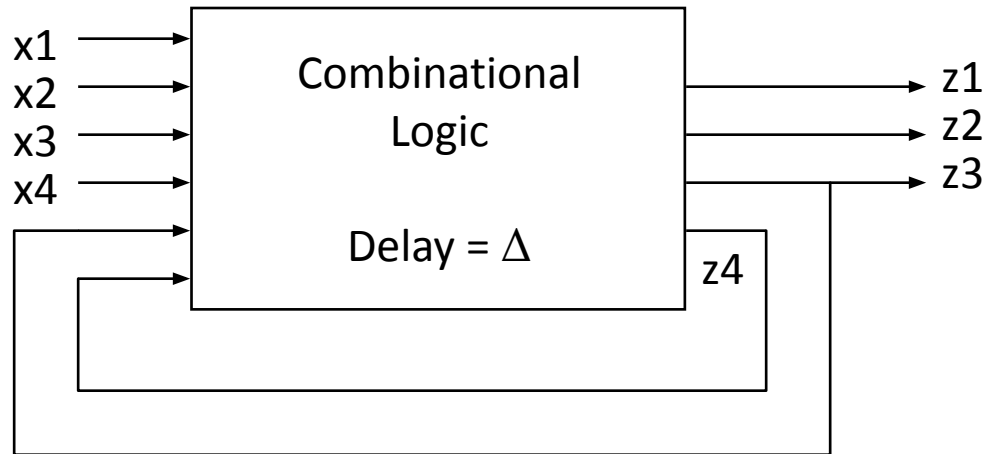

列出表达式: $z_3 = ?$

$$z_3(t+\Delta) = F(x_1(t), \dots, x_4(t), z_3(t), z_4(t))$$

Observations:


- z_3 and z_4 appear as both inputs and outputs.
- The “state” of variable z_3 (or z_4) at time $t+\Delta$ depends on its value at time t , i.e. $z_3(t+\Delta) = F(z_3(t))$, hence, circuit has memory.
- $z_3(t)$ and $z_4(t)$ are called state variables.

Next . . .


- ❖ Introduction to Sequential Circuits
- ❖ Synchronous versus Asynchronous
- ❖ Review Latches
- ❖ **Review Flip-Flops**
- ❖ **Characteristic Tables and Equations**

Flip-Flops (触发器)





 
- ❖ A **Flip-Flop** is a better memory element for synchronous circuits
- ❖ Solves the problem of latches in synchronous sequential circuits
- ❖ A **latch** is sensitive to the **level** of the clock
- ❖ However, a **flip-flop** is sensitive to the **edge** of the clock
- ❖ A flip-flop is called an **edge-triggered** memory element
- ❖ It changes its output value at the **edge** of the clock



如何实现边沿触发？

 

脉冲检测电路

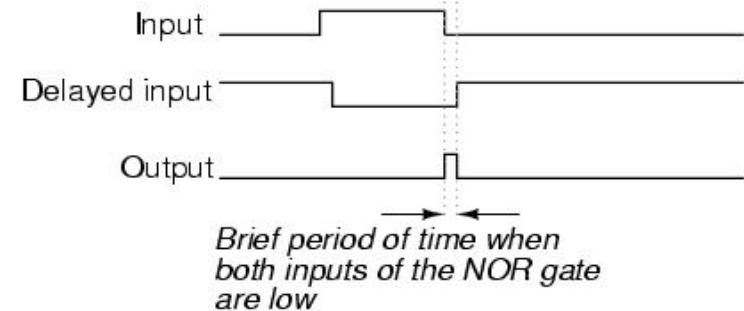    


Edge-Triggered D Flip-Flop

- ❖ Built using two latches in a **master-slave** configuration
- ❖ A master latch (D-type) receives external inputs
- ❖ A slave latch (SR-type) receives inputs from the master latch
- ❖ Only one latch is enabled at any given time

When **Clk=0**, the master is enabled and the D input is latched (slave disabled)

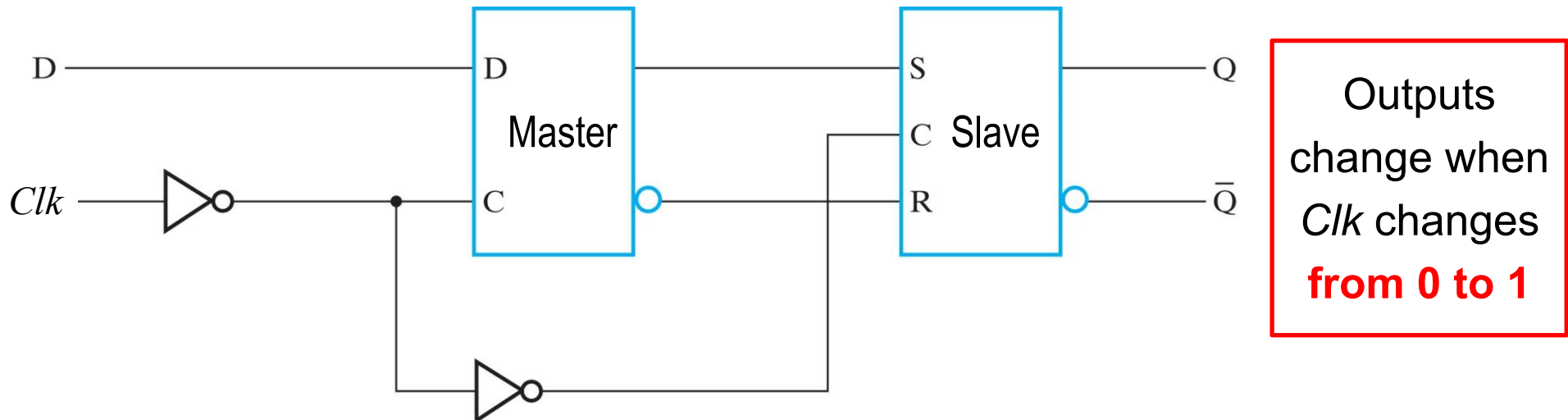When **Clk=1**, the slave is enabled to generate the outputs (master is disabled)




Negative Edge-Triggered D Flip-Flop

- ❖ Similar to positive edge-triggered flip-flop
- ❖ The first inverter at the Master C input is removed
- ❖ Only one latch is enabled at any given time

When **Clk=1**, the master is enabled and the D input is latched (slave disabled)

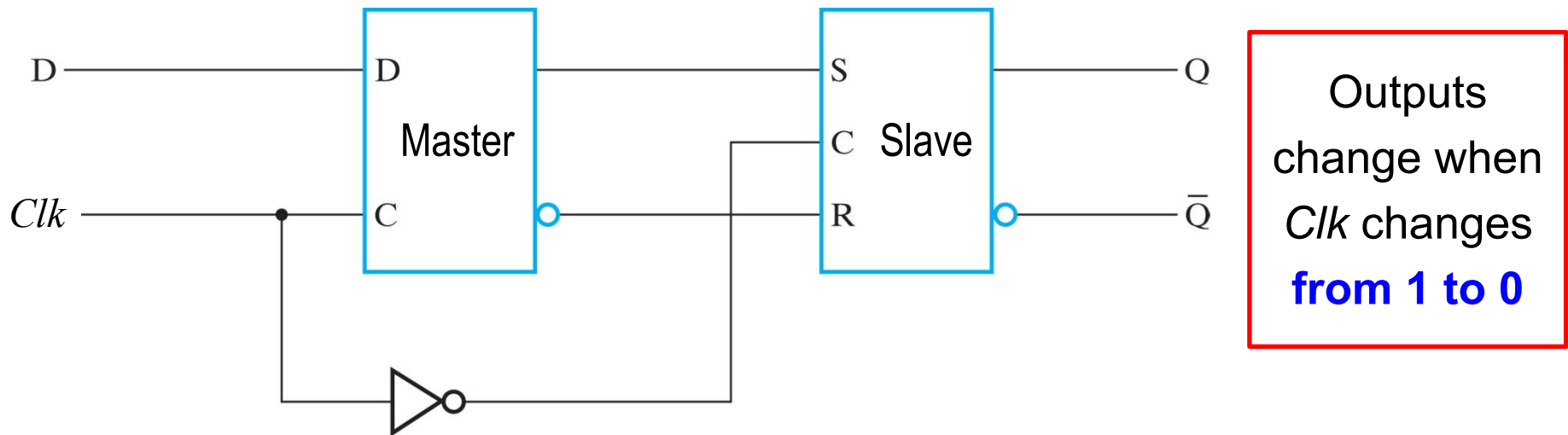When **Clk=0**, the slave is enabled to generate the outputs (master is disabled)



Edge-Triggered D Flip-Flop

- (1) Analyse the master-slave Flip-Flop
- (2) Please create the Truth Table

